

Switching Regulator IC Series

Bootstrap Circuit in the Buck Converter

This application note explains the step-up circuit using a bootstrap capacitor. In buck converters, this circuit is used when the high-side switch is the N-ch MOSFET.

1. Role of the bootstrap circuit in the buck converter

The configuration of the circuit in proximity to a buck converter depends on the polarity of the high-side switch.

When a P-ch MOSFET is used for the high-side switch, there are advantages over using a N-ch MOSFET, such as the capability of driving the switch with input voltage V_{IN} as the gate voltage, as well as voltage reduction and obtainment of the maximum duty. On the contrary, the use of a P-ch MOSFET requires a larger chip area for passing the same current.

The use of an N-ch MOSFET for the **high-side switch requires a gate voltage of $V_{IN} + V_{th}$** (threshold voltage of the N-ch MOSFET) or higher. A step-up circuit is required because the gate voltage is higher than V_{IN} . This circuit is configured with an internal diode and an external bootstrap capacitor (charge pump type). The total cost, including the cost of the external bootstrap capacitor, can be lowered because the chip area can be reduced compared with the P-ch MOSFET, as mentioned above.

2. Description of the charge pump operation

In the charge-pump-type step-up circuit, the essential parts include a diode and a capacitor (bootstrap capacitor). The diode is often built-in as an element in the IC, and only the bootstrap capacitor is connected externally.

Figure 1 shows an example of an actual circuit.

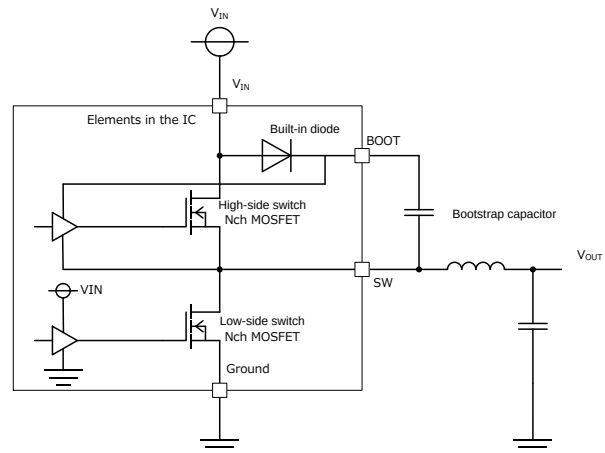


Figure 1. Example of a charge-pump-type step-up circuit

The voltages on the SW and BOOT pins in the example of Figure 1 are described as shown in Figure 2, where V_f is the forward direction voltage of the built-in diode.


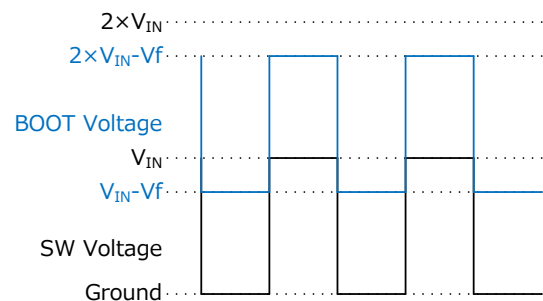


Figure 2. Voltages of SW and BOOT

When the SW voltage is low during the switching operations in Figure 2, the electric charge is stored in the capacitor from V_{IN} , thus resulting in the voltage of $V_{IN} - V_f$ across the capacitor. When the SW voltage is high, the BOOT voltage increases up to $2 \times V_{IN} - V_f$, and the built-in diode maintains the voltage at $2 \times V_{IN} - V_f$. Therefore, the BOOT voltage switches between $V_{IN} - V_f$ and $2 \times V_{IN} - V_f$ (Figure 3).

- When the SW voltage is low

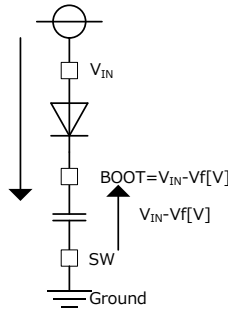Given that the V_{IN} voltage > BOOT voltage, a forward direction current flows in the diode. When SW = Ground, the BOOT voltage is $V_{IN} - V_f$ [V].



- When the SW voltage is high

Given that the V_{IN} voltage $\leq$ the BOOT voltage, no current flows in the diode. The voltage across the capacitor is maintained at $V_{IN} - V_f$ [V]. Therefore, the BOOT voltage is $2 \times V_{IN} - V_f$ [V] when SW = V_{IN} .


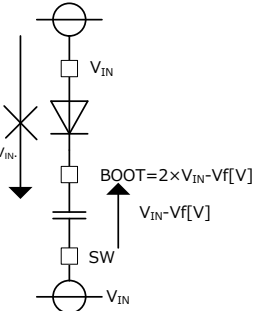



Figure 3. Charge-pump-type step-up circuit diagram

When this BOOT voltage is used as the gate voltage for the high-side N-ch MOSFET, you can obtain a voltage between the gate and the source (V_{GS}) that is sufficient to completely turn ON the MOSFET.

In this example, the anode of the built-in diode is obtained from V_{IN} , and the BOOT voltage can increase up to $2 \times V_{IN} - V_f$ as described in the calculation. It is possible that this BOOT voltage may exceed the breakdown voltage between the gate and source of the high-side N-ch MOSFET. Therefore, in designing products with a high input voltage, an internal power supply of approximately 5 V is connected to the anode so that the BOOT voltage is maintained below the breakdown voltage between the gate and the source (Figure 4).

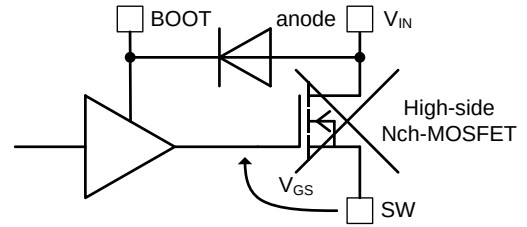

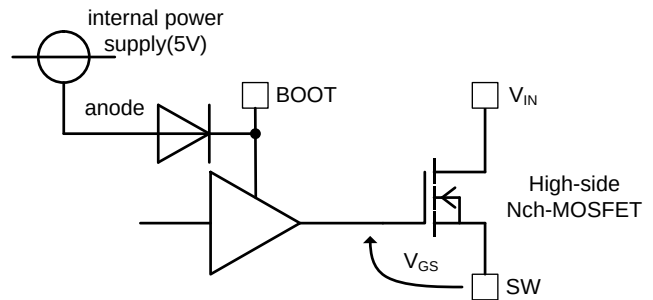When the anode of the diode is obtained from V_{IN} , the gate voltage of the high-side N-ch MOSFET is $V_{IN} - V_f$ [V] at maximum. When a high voltage is applied to V_{IN} and when the V_{GS} rating is exceeded, the high-side N-ch MOSFET will be destroyed.



When the anode of the diode is connected to an internal power supply of approximately 5 V, the gate voltage of the high-side N-ch MOSFET is $5 - V_f$ [V] at maximum. Therefore, the V_{GS} rating of the N-ch MOSFET will not be exceeded, and the high-side N-ch MOSFET can be protected.

Figure 4. Method that considers preventing the V_{GS} rating from being exceeded

3. Capacitance of the bootstrap capacitor

For the minimum capacitance of the bootstrap capacitors, follow the capacitance described in each data sheet. Use a small ceramic capacitor for the bootstrap capacitors. It is necessary to consider the DC bias characteristics of the ceramic capacitors and to confirm that the actual capacitance corresponds with the capacitance described in the data sheet.

The DC bias characteristics refer to the characteristics of variation in capacitance due to the DC voltage applied across the ceramic capacitor. Generally, the capacitance tends to decrease as the DC voltage increases. Furthermore, the variation in capacitance also depends on the size.

Figure 5 shows the examples of DC bias characteristics with different sizes.

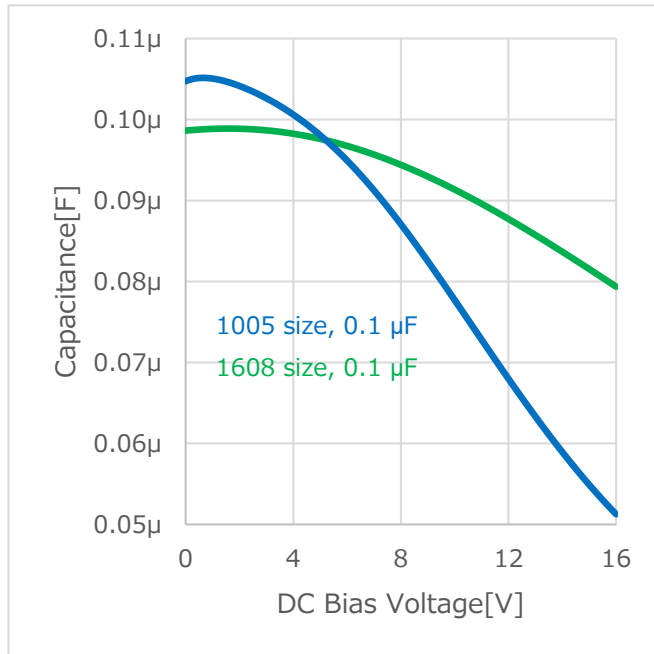


Figure 5. Examples of DC bias characteristics of ceramic capacitors

When 16 V is applied to the 1005 size ceramic capacitor, the actual capacitance falls significantly below the nominal value of 0.1 μF. Furthermore, approximately half of the nominal value remains. Although the minimum capacitance of the bootstrap capacitor varies with each IC, an excessively small capacitance may result in an electric charge that is insufficient for gate driving. The insufficient electric charge may lead to unstable gate driving and impair the operation.

However, we recommend the use of the minimum capacitor that satisfies the minimum capacitance because a larger size will affect the cost. On the contrary, an excessively large capacitance could delay the increase in the voltage across the capacitor and reduce the voltage for gate driving.

The adequate value of the capacitance can be obtained from the following equations. When the high-side N-ch MOSFET is ON, the electric charge stored in the bootstrap capacitor is consumed for the gate driving.

$$Q_{\text{LOSS}} = Q_G + I_{\text{BOOT}} \times \frac{D}{f} \quad (1)$$

Q_{LOSS} : Total electric charge consumed when N – ch MOSFET is ON

Q_G : Gate charge and electric charge lost in the internal circuit

I_{BOOT} : Current passing from the bootstrap capacitor

f : Switching frequency

D : Switching duty

Here, the relation of the variation in the voltage between BOOT and SW (ΔV_{BS}), the capacitance of the bootstrap capacitor (C_{BOOT}), and the Q_{LOSS} is expressed as follows.

$$C_{\text{BOOT}} \geq \frac{Q_{\text{LOSS}}}{\Delta V_{\text{BS}}} \quad (2)$$

Considering that it is desirable to maintain ΔV_{BS} at 0.1 V or below, the equation can be described as follows.

$$C_{\text{BOOT}} \geq \frac{Q_{\text{LOSS}}}{0.1} \quad (3)$$

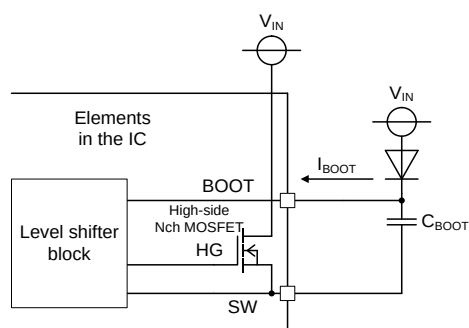


Figure 6. Circuit diagram required for C_{BOOT} determination

As an example, a calculation is performed with $Q_G = 10 \text{ nC}$, $I_{BOOT} = 10 \text{ nA}$, $D = 0.3$, and $f = 1 \text{ MHz}$. From Equation (1),

$$Q_{LOSS} = 10 \text{ nC} + 10 \text{ nA} \times \frac{0.3}{1 \text{ MHz}} \cong 10 \text{ nC}$$

When this value is substituted in Equation (3),

$$C_{BOOT} \geq \frac{10 \text{ nC}}{0.1} = 0.1 \mu\text{F}$$

Therefore, C_{BOOT} should be $0.1 \mu\text{F}$ or larger.

However, the capacitances described in the data sheet should be used because they are designed according to the results obtained from these equations.

Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products specified in this document are not designed to be radiation tolerant.
- 7) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 8) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 9) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 10) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 11) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 12) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 13) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<http://www.rohm.com/contact/>